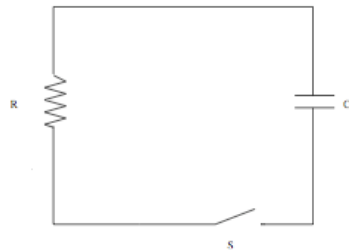


My Lectures from : Purcell Chapter 10.1-10.4;  
 Web Notes : Lecture Notes #4a,4b,4c  
 Other Notes: Capacitance; AC\_circuits


**Purcell Problems:**

- 10.3 Dipole moments
- 10.6 Parallel plate capacitor
- 10.14 Three capacitors


1. Consider the simplest RC circuit as shown below. Suppose that a charge  $Q_0$  is stored on the capacitor initially. Show that the total energy dissipated in the resistor after the switch is closed equals the energy that was stored in the capacitor before the switch was closed.



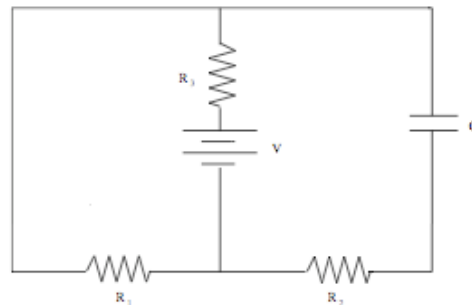2. Consider the circuit shown below. Suppose that the capacitor is initially discharged. The switch is closed at  $t = 0$  (circuit as shown). Find the charge  $I_B(t)$  through the battery, i.e., the middle branch, as a function of time, and the charge on the capacitor  $Q(t)$ .



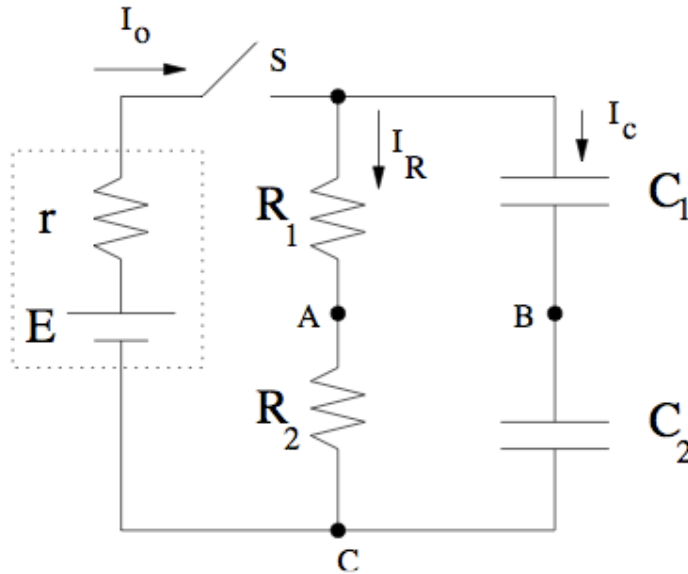3. A battery  $E$  with internal resistance  $r$ , two resistors  $R_1=10r$  and  $R_2=5r$  and two capacitors  $C_1$  and  $C_2$  with  $C_1=2C_2$  are arranged as shown below. The capacitors are initially uncharged. Express all your answers in terms of  $E$ ,  $r$ , and  $C_2$ .




- At  $t=0$ , the switch  $S$  is closed. What is the potential at  $A$  with respect to  $C$ , i.e.,  $V_{AC}=V_A-V_C$ , and what is the potential at  $B$  with respect to  $C$ , i.e.,  $V_{BC}=V_B-V_C$ ?
- After infinite time has elapsed (and with switch  $S$  remaining closed) what is  $V_{AC}=V_A-V_C$  and  $V_{BC}=V_B-V_C$ ?
- Write down a set of independent equations that will yield the solutions for the currents flowing in the three branches of the circuit, i.e.,  $I_0(t)$ ,  $I_R(t)$ ,  $I_c(t)$ . Do NOT solve them.

We now short-circuit points  $A$  and  $B$  by connecting them with a resistanceless conducting wire.

- Will there be any current flowing through it (yes/no) and in what direction?
- What will be the final  $V_{AC}=V_A-V_C$  and  $V_{BC}=V_B-V_C$ ?
- What is the total charge that passed through the short-circuiting wire? Is this consistent with the answer to (d)?

4. Consider the circuit below.

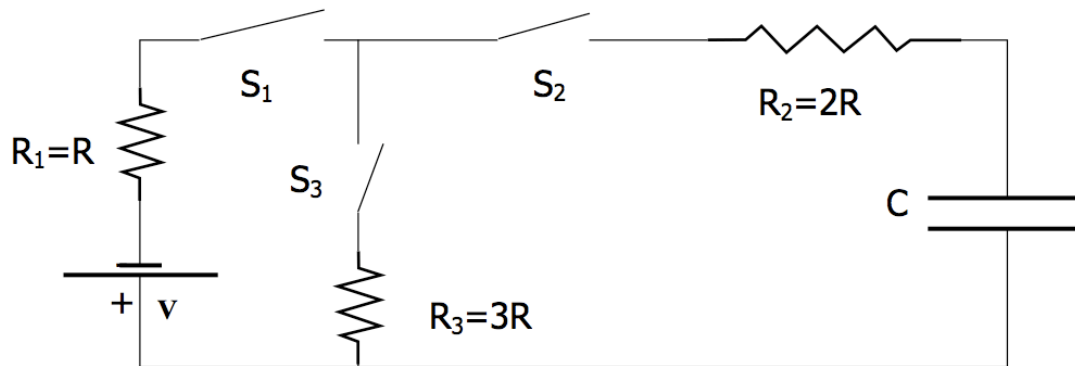

Initially all switches are open and the capacitor  $C$  is discharged.

- (a) At time  $t=t_0$ , we close  $S_1$  and  $S_2$  simultaneously.
- (b) At time  $t=t_1 \gg t_0$ , we close  $S_3$  (with  $S_1$  and  $S_2$  still closed)
- (c) At time  $t=t_2 \gg t_1$ , we open  $S_1$  ( $S_2$  and  $S_3$  still closed)

Sketch how the following quantities vary with time:

- (a)  $V_C$  (potential across the capacitor)
- (b)  $I_{R_2}$  (current through resistor  $R_2$ )
- (c)  $V_{R_3}$  (potential across resistor  $R_3$ )